

## Electric Circuits Auxilliary Items


### For Voltage-Current-Resistance Lab

(Tape the following into your Data section and complete.)

Data:

Resistor #1:  $R =$  \_\_\_\_\_  $\Omega$  (based on color code)

# of Batteries	$\Delta V$ (Volts)	I (Amps)
1		
2		
3		
4		

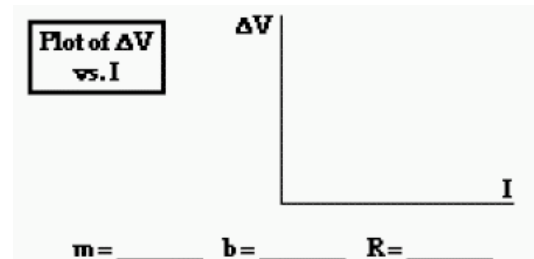

Resistor #2:  $R =$  \_\_\_\_\_  $\Omega$  (based on color code)

# of Batteries	$\Delta V$ (Volts)	I (Amps)
1		
2		
3		
4		

