


Combination Circuits Lesson Notes

Learning Outcomes


- What are the main mathematical patterns and relationships associated with combination circuits?
- How can one analyze such circuits?

What is a Combination Circuit?

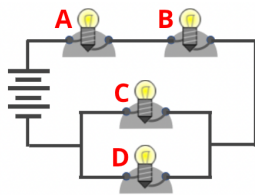
A combination circuit includes devices that are connected by a combination of series and parallel connections.



Series: A, B Parallel: C, D

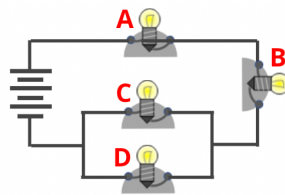

Series: A, B Parallel: C, D

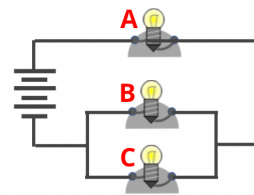


Series: A Parallel: B, C

Equivalent Resistance

The collection of resistors act together to create an overall total resistance known as the **equivalent resistance** (R_{eq}).

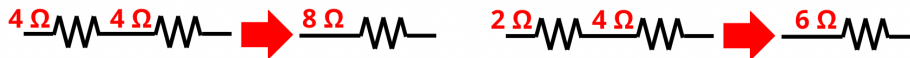For series connections: $R_{eq} = R_1 + R_2 + R_3 + \dots$



For parallel connections: $1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3 + \dots$



$$1/R_{eq} = 1/(4) + 1/(4) = 0.50$$


$$R_{eq} = 1/(0.50) = 2.0$$

$$1/R_{eq} = 1/(12) + 1/(6) = 0.25$$

$$R_{eq} = 1/(0.25) = 4.0$$


R_{eq} for a Combination Circuit

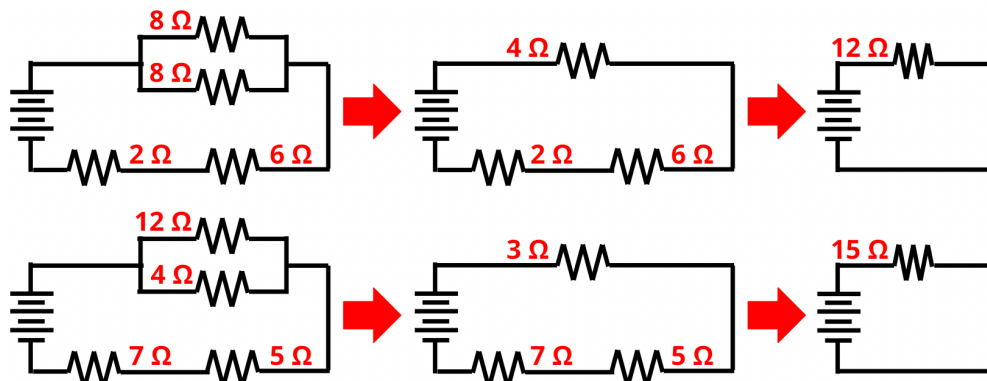The equivalent resistance of a combination circuit can be determined by reducing groups of resistors to a single resistance in a stepwise fashion, beginning with the branched resistors.



Voltage Drops (ΔV)


- For the *branched* resistors (R_1 and R_2), the voltage drop is the same. So $\Delta V_1 = \Delta V_2$.
- For all resistors, the voltage drop can be calculated using $\Delta V = I \cdot R$. So ...
 $\Delta V_1 = I_1 \cdot R_1$ $\Delta V_2 = I_2 \cdot R_2$ $\Delta V_3 = I_3 \cdot R_3$ etc.
- Counting the branches as a single drop, the sum of all voltage drops equals the battery voltage.
- For the given circuit: $\Delta V_{\text{battery}} = \Delta V_{\text{branches}} + \Delta V_3 + \Delta V_4$

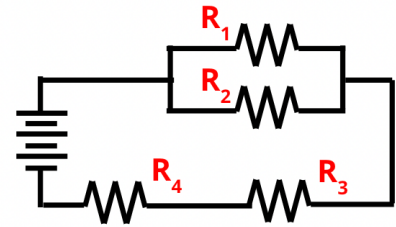

Current (I)


For combination circuits:

- The current in the battery is the same as the current in every resistor located outside the branches. For the given circuit: $I_{\text{battery}} = I_3 = I_4$
- The current outside the branches is equal to the sum of the branch currents. For the given circuit: $I_{\text{battery}} = I_1 + I_2$
- For any resistor, the current can be calculated using $\Delta V = I \cdot R$. So ... $I_1 = \Delta V_1 / R_1$ $I_2 = \Delta V_2 / R_2$ $I_3 = \Delta V_3 / R_3$ etc.
- Branches having equal resistance will have equal current values.

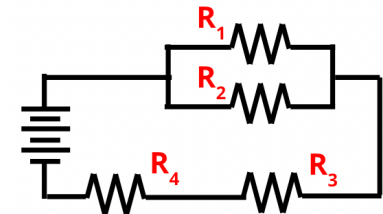


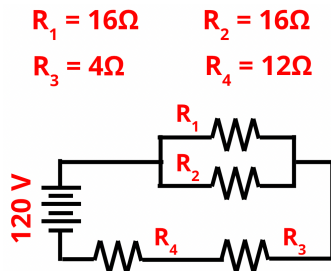Examples

Analyze the following two combination circuits. Fill in all blanks.



$R_{\text{eq}} =$ _____	$I_{\text{battery}} =$ _____
$I_1 =$ _____	$\Delta V_1 =$ _____
$I_2 =$ _____	$\Delta V_2 =$ _____
$I_3 =$ _____	$\Delta V_3 =$ _____
$I_4 =$ _____	$\Delta V_4 =$ _____

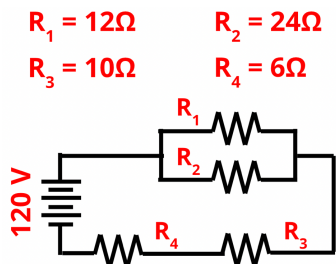

$R_{\text{eq}} =$ _____	$I_{\text{battery}} =$ _____
$I_1 =$ _____	$\Delta V_1 =$ _____
$I_2 =$ _____	$\Delta V_2 =$ _____
$I_3 =$ _____	$\Delta V_3 =$ _____
$I_4 =$ _____	$\Delta V_4 =$ _____