


## Parallel Circuit Relationships Lesson Notes

### Learning Outcomes

- What are the important mathematical patterns and relationships associated with parallel circuits?
- How do you use these relationships?

### What is a Parallel Circuit?

#### Parallel Circuit

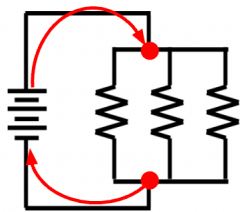


Branches!!!  
Multiple pathways.  
Charge passes through just one of the resistors.

#### For Parallel Circuits:



As the number of resistors increases ...  
... total resistance decreases  
... current increases, and  
Removing a bulb from its socket has no effect on the other bulbs.
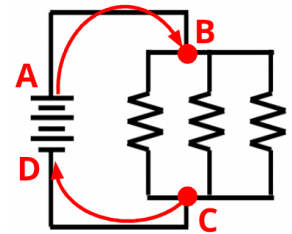
### Voltage Drops Across the Branches

- Charge traversing *the loop* of a parallel circuit will only pass through one branch before returning to the battery.
- There is a voltage gain in the battery and a voltage drop in the branches. These must be equal.


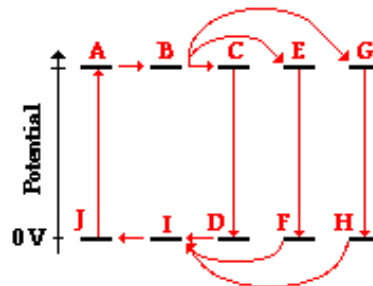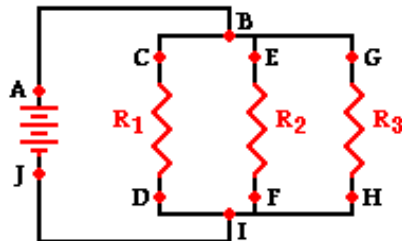
$$\Delta V_{\text{battery}} = \Delta V_1 = \Delta V_2 = \Delta V_3 = \dots$$




### Current

- The current outside the branches is equal to the sum of the branch currents.  $I_{\text{battery}} = I_1 + I_2 + I_3 + \dots$
- Current can be calculated using:

$$I_1 = \frac{\Delta V}{R_1} \quad I_2 = \frac{\Delta V}{R_2} \quad I_3 = \frac{\Delta V}{R_3}$$

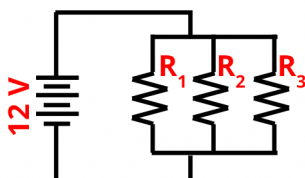
**Example:** Three resistors are connected to a 12 V battery.  
 $R_1 = 2 \Omega$ ,  $R_2 = 6 \Omega$ , and  $R_3 = 4 \Omega$ . Determine  $I_1$ ,  $I_2$ , and  $I_3$ .



$$I_1 = (12 \text{ V}) / (2 \Omega) = 6 \text{ A}$$

$$I_2 = (12 \text{ V}) / (6 \Omega) = 2 \text{ A}$$
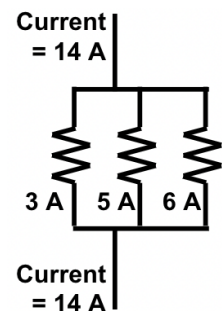
$$I_3 = (12 \text{ V}) / (4 \Omega) = 3 \text{ A}$$




## Equivalent Resistance

The **equivalent resistance** ( $R_{eq}$ ) of a multiple-resistor circuit is the amount of resistance a single resistor must have to match the effect of the collection of resistors.

For parallel circuits, the equivalent resistance is calculated as
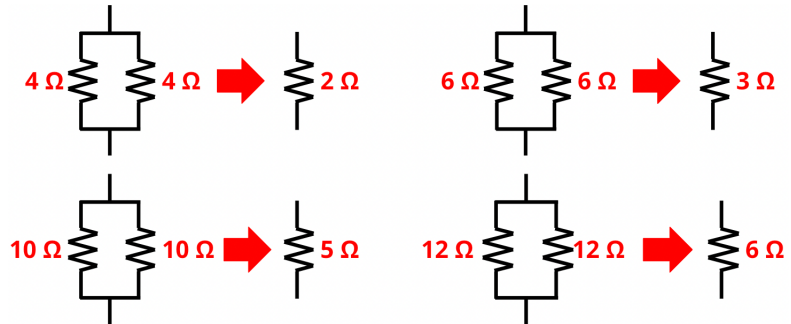
$$1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3 + \dots$$



$R_1$ ( $\Omega$ )	$R_2$ ( $\Omega$ )	$R_3$ ( $\Omega$ )	$1/R_1 + 1/R_2 + 1/R_3$	$R_{eq}$ ( $\Omega$ )
4.0	4.0	–	$1/(4.0) + 1/(4.0) = 0.50$	2.0
12	12	–	$1/(12) + 1/(12) = 0.1666\dots$	6.0
12	12	12	$1/(12) + 1/(12) + 1/(12) = 0.25$	4.0
2.0	3.0	4.0	$1/(2.0) + 1/(3.0) + 1/(4.0) = 1.083$	0.92
4.5	6.6	5.1	$1/(4.5) + 1/(6.6) + 1/(5.1) = 0.5698$	1.75


The  $R_{eq}$  value is always smaller than the smallest R value. Adding a resistor in a parallel branch always makes the overall resistance less.

## Concept Practice

Identify and explain the answers to the following Concept Questions:

Three identical light bulbs are connected to a battery. P, Q, X, Y and Z represent locations along the circuit. Which one of the statements is true?

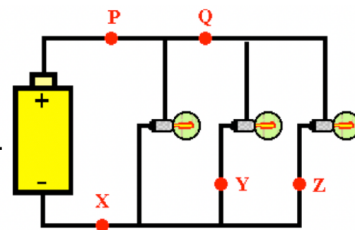- The current at Y is greater than the current at Q.
- The current at Y is greater than the current at P.
- The current at Y is greater than the current at Z.
- The current at P is greater than the current at Q.
- The current at Q is greater than the current at P.
- The current is the same at all locations.



Which adjustments could be made to the circuit that would increase the current at X? Identify all that apply.

- Increase the resistance of one of the bulbs.
- Increase the resistance of two of the bulbs.
- Decrease the resistance of two of the bulbs.
- Increase the voltage of the battery.
- Decrease the voltage of the battery.
- Remove one of the bulbs.

